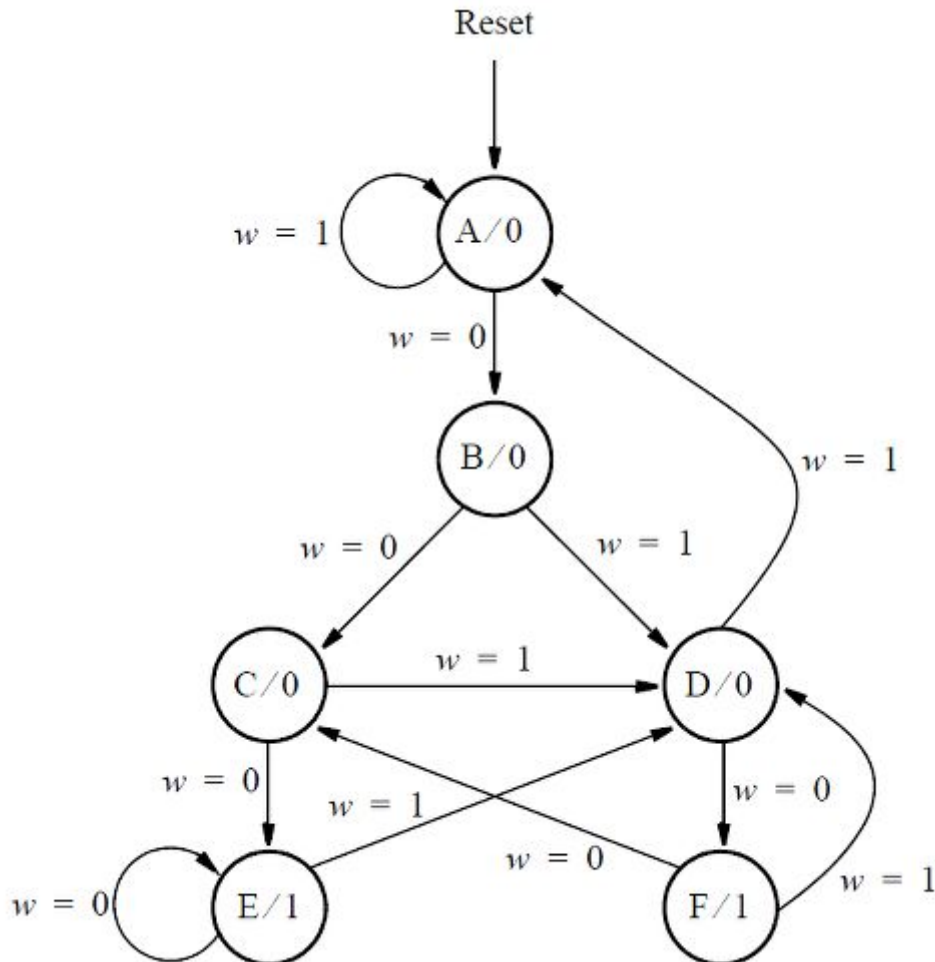


# Exams/m2014 q6c

Consider the state machine shown below, which has one input  $w$  and one output  $z$ .



For this part, assume that a one-hot code is used with the state assignment  $y[6:1] = 000001, 000010, 000100, 001000, 010000, 100000$  for states  $A, B, \dots, F$ , respectively.

Write a logic expression for the next-state signals  $Y2$  and  $Y4$ . (Derive the logic equations by inspection assuming a one-hot encoding. The testbench will test with non-one hot inputs to make sure you're not trying to do something more complicated).

這題蠻單純的，因為是one-hot所以很容易在state machine上觀察跳動  
題目裡要

找Y2也就是next state為B，總共只有一個箭頭會跳進B，條件是current state A 且收到  $w=0$

找Y4也就是next state為D，從current state {B C E F}收到 $w=1$ 之後可以跳進D

把這幾個bit的相對位置找出來寫一寫簡單邏輯就成功了。

```
module top_module (
    input [6:1] y,
    input w,
    output Y2,
    output Y4);
```

```
//Y2=B: 1 arrow points to state_B: CurrStateA with w=0
//Y4=D: 4 arrow points to state_D: CurrState= {B C E F} with w=1
//      B=y2      y4=D
// curr  w=0 w=1  w=0 w=1
//-----
//A 000001  x  x  x
//B 000010  Y  x  x  Y
//C 000100  x  x  x  Y
//D 001000  x  x  x
//E 010000  x  x  x  Y
//F 100000  x  x  x  Y
```

```
assign Y2 = ~w & y[1];
assign Y4 = w & (y[2]|y[3]|y[5]|y[6]);
```

```
endmodule
```