


Fsm serial

In many (older) serial communications protocols, each data byte is sent along with a start bit and a stop bit, to help the receiver delimit bytes from the stream of bits. One common scheme is to use one start bit (0), 8 data bits, and 1 stop bit (1). The line is also at logic 1 when nothing is being transmitted (idle).


Design a finite state machine that will identify when bytes have been correctly received when given a stream of bits. It needs to identify the start bit, wait for all 8 data bits, then verify that the stop bit was correct. If the stop bit does not appear when expected, the FSM must wait until it finds a stop bit before attempting to receive the next byte.

Some timing diagrams

Error-free:

 

 Stop bit not found. First byte is discarded:



```
module top_module(  
    input clk,  
    input in,  
    input reset,    // Synchronous reset  
    output done  
);  
    parameter WAIT = 4'b0001;  
    parameter DATA = 4'b0010;  
    parameter CHECK = 4'b0100;  
    parameter ERR = 4'b1000;  
    reg [3:0] curr_state;  
    reg [3:0] next_state;  
    wire data_to_check;  
    wire check2wait;  
    always @ (*) begin  
        case(curr_state)
```

```

    WAIT :next_state=(~in)?DATA:WAIT;
    DATA :next_state=(data_to_check)?CHECK:DATA;
    CHECK:next_state=( in)?WAIT:ERR;
    ERR :next_state=( in)?WAIT:ERR;
    default:next_state=curr_state;
endcase
end
always@(posedge clk)begin
    if(reset)begin
        curr_state<=WAIT;
    end
    else begin
        curr_state<=next_state;
    end
end
end

```

```

reg [2:0] cnt;
assign data_to_check = (curr_state==DATA) & (cnt==3'd7);
always@(posedge clk)begin
    if(reset)begin
        cnt<=3'd0;
    end
    else if(data_to_check)begin
        cnt<=3'd0;
    end
    else if(curr_state==DATA)begin
        cnt<= cnt+3'd1;
    end
end
end

```

```

assign check2wait = (curr_state==CHECK) & in;

```

```

always@(posedge clk)begin
    if(reset)begin
        done<=1'b0;
    end
    else if(done)begin
        done<=1'b0;
    end
    else if(check2wait)begin
        done<=1'b1;
    end
end
end

```

```

endmodule

```

Fsm serialdata


See also: [Serial receiver](#)

Now that you have a finite state machine that can identify when bytes are correctly received in a serial bitstream, add a datapath that will output the correctly-received data byte. `out_byte` needs to be valid when `done` is 1, and is don't-care otherwise.

Note that the serial protocol sends the *least* significant bit first.

Some timing diagrams

Error-free:

 

```
module top_module(  
    input clk,  
    input in,  
    input reset, // Synchronous reset  
    output [7:0] out_byte,  
    output done  
); //  
  
    parameter WAIT = 4'b0001;  
    parameter DATA = 4'b0010;  
    parameter CHECK = 4'b0100;  
    parameter ERR = 4'b1000;  
    reg [3:0] curr_state;  
    reg [3:0] next_state;  
    wire data_to_check;  
    wire check2wait;  
    always @ (*) begin  
        case(curr_state)  
            WAIT :next_state=(~in)?DATA:WAIT;  
            DATA :next_state=(data_to_check)?CHECK:DATA;  
            CHECK:next_state=( in)?WAIT:ERR;  
            ERR :next_state=( in)?WAIT:ERR;  
            default:next_state=curr_state;  
        endcase  
    end  
    always@(posedge clk)begin  
        if(reset)begin
```

```

    curr_state<=WAIT;
end
else begin
    curr_state<=next_state;
end
end
end

```

```

reg [2:0] cnt;
assign data_to_check = (curr_state==DATA) & (cnt==3'd7);
always@(posedge clk)begin
    if(reset)begin
        cnt<=3'd0;
    end
    else if(data_to_check)begin
        cnt<=3'd0;
    end
    else if(curr_state==DATA)begin
        cnt<= cnt+3'd1;
    end
end
end

```

```

assign check2wait = (curr_state==CHECK) & in;

```

```

always@(posedge clk)begin
    if(reset)begin
        done<=1'b0;
    end
    else if(done)begin
        done<=1'b0;
    end
    else if(check2wait)begin
        done<=1'b1;
    end
end
end

```

```

reg [7:0] shift_reg;
always @(posedge clk )begin
    if(reset)begin
        shift_reg <= 8'b0;
    end
    else if(curr_state==DATA)begin
        shift_reg = {in,shift_reg[7:1]};
    end
end
end

```

```

    assign out_byte = shift_reg;
    // New: Datapath to latch input bits.

```

```

endmodule

```

Fsm serialdp

See also: [Serial receiver and datapath](#)

We want to add parity checking to the serial receiver. Parity checking adds one extra bit after each data byte. We will use odd parity, where the number of 1s in the 9 bits received must be odd. For example, 101001011 satisfies odd parity (there are 5 1s), but 001001011 does not.

Change your FSM and datapath to perform odd parity checking. Assert the done signal only if a byte is correctly received *and* its parity check passes. Like the [serial receiver FSM](#), this FSM needs to identify the start bit, wait for all 9 (data and parity) bits, then verify that the stop bit was correct. If the stop bit does not appear when expected, the FSM must wait until it finds a stop bit before attempting to receive the next byte.


You are provided with the following module that can be used to calculate the parity of the input stream (It's a TFF with reset). The intended use is that it should be given the input bit stream, and reset at appropriate times so it counts the number of 1 bits in each byte.

```
module parity (  
    input clk,  
    input reset,  
    input in,  
    output reg odd);  
  
    always @(posedge clk)  
        if (reset) odd <= 0;  
        else if (in) odd <= ~odd;  
  
endmodule
```

Note that the serial protocol sends the least significant bit first, and the parity bit after the 8 data bits.

Some timing diagrams

 No framing errors. Odd parity passes for first byte, fails for second byte.



```
module top_module(  
    input clk,
```

```

input in,
input reset, // Synchronous reset
output [7:0] out_byte,
output done
); //
    parameter WAIT = 5'b00001;
parameter DATA = 5'b00010;
parameter CHECK = 5'b00100;
parameter PAR_CK= 5'b01000;
parameter ERR = 5'b10000;
reg [4:0] curr_state;
reg [4:0] next_state;
wire data_to_parcheck;
wire par_ok;
wire check2wait;
always @ (*) begin
    case(curr_state)
        WAIT :next_state=(~in)?DATA:WAIT;
        DATA :next_state=(data_to_parcheck)?PAR_CK:DATA;
        PAR_CK:next_state=(par_ok)?CHECK:ERR;
        CHECK :next_state=( in)?WAIT:ERR;
        ERR :next_state=( in)?WAIT:ERR;
        default:next_state=curr_state;
    endcase
end
always@(posedge clk)begin
    if(reset)begin
        curr_state<=WAIT;
    end
    else begin
        curr_state<=next_state;
    end
end

reg [2:0] cnt;
assign data_to_parcheck = (curr_state==DATA) & (cnt==3'd7);
always@(posedge clk)begin
    if(reset)begin
        cnt<=3'd0;
    end
    else if(data_to_parcheck)begin
        cnt<=3'd0;
    end
    else if(curr_state==DATA)begin
        cnt<= cnt+3'd1;
    end
end

assign check2wait = (curr_state==CHECK) & in;

always@(posedge clk)begin
    if(reset)begin
        done<=1'b0;
    end
    else if(done)begin

```

```

        done<=1'b0;
    end
    else if(check2wait)begin
        done<=1'b1;
    end
end

reg [7:0] shift_reg;
always @(posedge clk )begin
    if(reset)begin
        shift_reg <= 8'b0;
    end
    else if (curr_state==WAIT & ~in)begin
        shift_reg <= 8'b0;
    end
    else if(curr_state==DATA)begin
        shift_reg = {in,shift_reg[7:1]};
    end
end

assign par_ok = (curr_state==PAR_CHK) & (^{in,shift_reg[7:0]});

    assign out_byte = shift_reg;

endmodule

```