 
 


# Exams/2014 q3fsm

Consider a finite state machine with inputs  $s$  and  $w$ . Assume that the FSM begins in a reset state called  $A$ , as depicted below. The FSM remains in state  $A$  as long as  $s = 0$ , and it moves to state  $B$  when  $s = 1$ . Once in state  $B$  the FSM examines the value of the input  $w$  in the next three clock cycles. If  $w = 1$  in exactly two of these clock cycles, then the FSM has to set an output  $z$  to 1 in the following clock cycle. Otherwise  $z$  has to be 0. The FSM continues checking  $w$  for the next three clock cycles, and so on. The timing diagram below illustrates the required values of  $z$  for different values of  $w$ .

Use as few states as possible. Note that the  $s$  input is used only in state  $A$ , so you need to consider just the  $w$  input.



FSM還算單純 主要是在狀態B要另外設一個**counter** 123 123一直跑一直跑 (每次數到3歸零 每次數到3歸零)

處理 $z$ 的話 很顯然要紀錄數3個cycle總共收到了幾個 $w$

我的做法是數前2個cycle搭配第3個cycle的 $w$ 來做一個 $z\_trigger$ 訊號 條件如下:

- 1.前2個cycle總共收到1個 $w$  此時第3cycle,  $w$ 必需=1 才有接下來的 $z$
- 2.前2個cycle總共收到2個 $w$  此時第3cycle,  $w$ 要等於0 才有接下來的 $z$

我們的 $z\_trigger$ 就設成上面兩個條件的任一個成立

剩下的code就很簡單就能code出來了

```
module top_module (
    input clk,
    input reset, // Synchronous reset
    input s,
    input w,
    output z
);
    parameter A = 1'b0;
    parameter B = 1'b1;

    reg curr_state, next_state;
```

```

always @ (posedge clk)begin
    if(reset)begin
        curr_state <= A;
    end
    else begin
        curr_state <= next_state;
    end
end

always @ (*) begin
    case(curr_state)
        A: next_state = s? B : A;
        B: next_state = B;
    endcase
end

reg [1:0] loop_cnt;
wire    set_loop_cnt = ((curr_state==A) & (next_state==B))|
                    ((curr_state==B) & (loop_cnt==2'd3)); //1 2 3 1 2 3 1 2 3

always @ (posedge clk)begin
    if(reset)begin
        loop_cnt <= 2'd0;
    end
    else if(set_loop_cnt)begin
        loop_cnt <= 2'd1;
    end
    else if(curr_state==B)begin
        loop_cnt <= loop_cnt + 2'd1;
    end
end

reg [1:0] w_cnt;
always @ (posedge clk)begin
    if(reset)begin
        w_cnt <= 2'd0;
    end
    else if(set_loop_cnt) begin
        w_cnt <= 2'd0;
    end
    else if(curr_state==B & w==1'b1)begin
        w_cnt <= w_cnt + 2'd1;
    end
end

wire z_trigger;
assign z_trigger = ((w_cnt == 2'd1)& ((loop_cnt==2'd3) & w)) |
                    ((w_cnt == 2'd2)& ((loop_cnt==2'd3) & ~w));
reg z_valid;
always @ (posedge clk)begin
    if(reset)begin
        z_valid <= 1'b0;
    end
    else if (z_trigger)begin
        z_valid <= 1'b1;
    end
    else if(set_loop_cnt)begin

```

```
        z_valid <= 1'b0;
    end
end
assign z = (loop_cnt==2'd1) & z_valid;

endmodule
```