

Hadd

Create a half adder. A half adder adds two bits (with no carry-in) and produces a sum and carry-out.

```
module top_module(  
    input a, b,  
    output cout, sum );  
    assign {cout,sum} = a+b;  
  
endmodule
```

Fadd

Create a full adder. A full adder adds three bits (including carry-in) and produces a sum and carry-out.

```
module top_module(  
    input a, b, cin,  
    output cout, sum );  
  
    assign{cout,sum}=a+b+cin;  
  
endmodule
```

Adder3

Now that you know how to build a [full adder](#), make 3 instances of it to create a 3-bit binary ripple-carry adder. The adder adds two 3-bit numbers and a carry-in to produce a 3-bit sum and carry out. To encourage you to actually instantiate full adders, also output the carry-out from *each* full adder in the ripple-carry adder. cout[2] is the final carry-out from the last full adder, and is the carry-out you usually see.

```
module top_module(  
    input [2:0] a, b,  
    input cin,  
    output [2:0] cout,  
    output [2:0] sum );  
  
    wire carry0, carry1, carry2;  
    wire sum0, sum1, sum2;  
    assign {carry0,sum0}=a[0]+b[0]+cin;  
    assign {carry1,sum1}=a[1]+b[1]+carry0;
```


```
assign {carry2,sum2}=a[2]+b[2]+carry1;
```

```
assign sum = {sum2,sum1,sum0};  
assign cout = {carry2,carry1,carry0};
```

```
endmodule
```

Exams/m2014 q4j

Implement the following circuit:

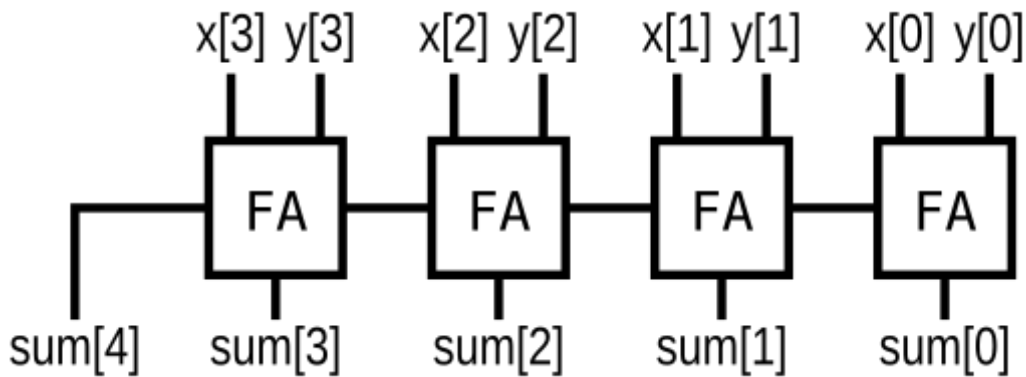

("FA" is a full adder)

```
module top_module (  
    input [3:0] x,  
    input [3:0] y,  
    output [4:0] sum);  
  
    assign sum = {1'b0,x}+{1'b0,y};  
endmodule
```

Exams/ece241 2014 q1c

Assume that you have two 8-bit 2's complement numbers, $a[7:0]$ and $b[7:0]$. These numbers are added to produce $s[7:0]$. Also compute whether a (signed) overflow has occurred.

A *signed* overflow occurs when adding two positive numbers produces a negative result, or adding two negative numbers produces a positive result. There are several methods to detect overflow: It could be computed by comparing the signs of the input and output numbers, or derived from the carry-out of bit n and $n-1$.

```
module top_module (  
    input [7:0] a,  
    input [7:0] b,  
    output [7:0] s,  
    output overflow  
); //  
  
    assign s = a+b;  
        //pos 0  neg1 : adding two positive numbers but produces a negative outcome  
        //          adding two negative numbers but produces a positive outcome  
        //          0  0  1  1  1  0  
    assign overflow = ~a[7]&~b[7]&s[7] | a[7]&b[7]&~s[7];  
  
endmodule
```

Adder100

Create a 100-bit binary adder. The adder adds two 100-bit numbers and a carry-in to produce a 100-bit sum and carry out.

```
module top_module(  
    input [99:0] a, b,  
    input cin,  
    output cout,  
    output [99:0] sum );  
    assign {cout,sum} = a+b+cin;  
  
endmodule
```

Bcdadd4

You are provided with a BCD (binary-coded decimal) one-digit adder named `bcd_fadd` that adds two BCD digits and carry-in, and produces a sum and carry-out.

```
module bcd_fadd {  
    input [3:0] a,  
    input [3:0] b,  
    input      cin,  
    output     cout,  
    output [3:0] sum );
```

Instantiate 4 copies of `bcd_fadd` to create a 4-digit BCD ripple-carry adder. Your adder should add two 4-digit BCD numbers (packed into 16-bit vectors) and a carry-in to produce a 4-digit sum and carry out.

- The BCD representation for the 5-digit decimal number 12345 is `20'h12345`. This is not the same as `14'd12345` (which is `14'h3039`).
- The circuit is structured just like a binary ripple-carry adder, except the adders are base-10 rather than base-2.

```
module top_module(  
    input [15:0] a, b,  
    input cin,  
    output cout,  
    output [15:0] sum );  
  
    wire c0,c1,c2;  
  
    bcd_fadd add0(a[ 3: 0],b[ 3: 0], cin,  c0,sum[ 3: 0]);  
    bcd_fadd add1(a[ 7: 4],b[ 7: 4], c0,  c1,sum[ 7: 4]);  
    bcd_fadd add2(a[11: 8],b[11: 8], c1,  c2,sum[11:08]);  
    bcd_fadd add3(a[15:12],b[15:12], c2, cout,sum[15:12]);  
endmodule
```