 


# Exams/2013 q2afsm

Consider the FSM described by the state diagram shown below:



This FSM acts as an arbiter circuit, which controls access to some type of resource by three requesting devices. Each device makes its request for the resource by setting a signal  $r[i] = 1$ , where  $r[i]$  is either  $r[1]$ ,  $r[2]$ , or  $r[3]$ . Each  $r[i]$  is an input signal to the FSM, and represents one of the three devices. The FSM stays in state A as long as there are no requests. When one or more request occurs, then the FSM decides which device receives a grant to use the resource and changes to a state that sets that device's  $g[i]$  signal to 1. Each  $g[i]$  is an output from the FSM. There is a priority system, in that device 1 has a higher priority than device 2, and device 3 has the lowest priority. Hence, for example, device 3 will only receive a grant if it is the only device making a request when the FSM is in state A. Once a device,  $i$ , is given a grant by the FSM, that device continues to receive the grant as long as its request,  $r[i] = 1$ .

Write complete Verilog code that represents this FSM. Use separate always blocks for the state table and the state flip-flops, as done in lectures. Describe the FSM outputs,  $g[i]$ , using either continuous assignment statement(s) or an always block (at your discretion). Assign any state codes that you wish to use.

這是一個有優先權的FSM, r1有最高權限, r3最小。如果搶到權限後可以一直佔住grant持續使用。既然是有優先順序, 必須在next state裡寫出硬體上有順序性的if(第一順位), else if(第二順位), else if(第三順位)....

```
module top_module (
    input clk,
    input resetn,    // active-low synchronous reset
    input [3:1] r,   // request
    output [3:1] g   // grant
);
    parameter A = 2'd0;
    parameter B = 2'd1;
    parameter C = 2'd2;
    parameter D = 2'd3;

    reg [1:0] curr_state;
    reg [1:0] next_state;

    always @ (posedge clk) begin
        if(~resetn)begin
            curr_state <= A;
        end
        else begin
            curr_state <= next_state;
        end
    end

    always @ (*) begin
        case(curr_state)
            A: if (r[1]) begin
                next_state = B;
            end
            else if(r[2]) begin
                next_state = C;
            end
            else if(r[3]) begin
                next_state = D;
            end
            else begin
                next_state=A;
            end

            B: next_state = r[1]? B:A;
            C: next_state = r[2]? C:A;
            D: next_state = r[3]? D:A;
        endcase
    end

    assign g[1] = curr_state==B;
    assign g[2] = curr_state==C;
    assign g[3] = curr_state==D;

endmodule
```