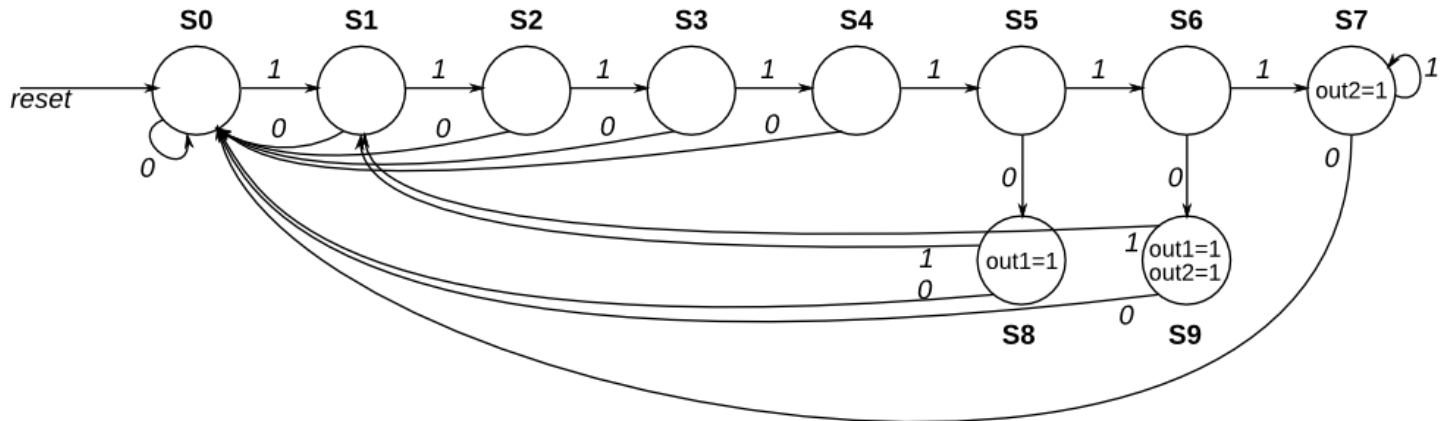


# Fsm onehot

Given the following state machine with 1 input and 2 outputs:



Suppose this state machine uses one-hot encoding, where state[0] through state[9] correspond to the states S0 through S9, respectively. The outputs are zero unless otherwise specified.

Implement the **state transition logic** and **output logic** portions of the state machine (but not the state flip-flops). You are given the current state in state[9:0] and must produce next\_state[9:0] and the two outputs. Derive the logic equations by inspection assuming a one-hot encoding. (The testbench will test with non-one hot inputs to make sure you're not trying to do something more complicated).

```
module top_module(  
    input in,  
    input [9:0] state,  
    output [9:0] next_state,  
    output out1,  
    output out2);  
  
    always @(*)begin  
        next_state[0] = ~in & (!state[9:7],state[4:0]);  
        next_state[1] = in & state[0] | (!state[9:8] & in);  
        next_state[2] = in & state[1];  
        next_state[3] = in & state[2];  
        next_state[4] = in & state[3];  
        next_state[5] = in & state[4];  
        next_state[6] = in & state[5];  
        next_state[7] = in & (!state[7:6]);  
        next_state[8] = ~in & state[5];  
        next_state[9] = ~in & state[6];  
    end  
  
    assign out1 = state[8] | state[9];  
    assign out2 = state[7] | state[9];  
endmodule
```
