

# Count clock


← [countbcd](#) ✓ Previous

Next [shift4](#) ○ →

Create a set of counters suitable for use as a 12-hour clock (with am/pm indicator). Your counters are clocked by a fast-running `clk`, with a pulse on `ena` whenever your clock should increment (i.e., once per second).

`reset` resets the clock to 12:00 AM. `pm` is 0 for AM and 1 for PM. `hh`, `mm`, and `ss` are two BCD (Binary-Coded Decimal) digits each for hours (01-12), minutes (00-59), and seconds (00-59). Reset has higher priority than enable, and can occur even when not enabled.

 The following timing diagram shows the rollover behaviour from 11:59:59 AM to 12:00:00 PM and the synchronous reset and enable behaviour.



[https://hdlbits.01xz.net/wiki/Count\\_clock](https://hdlbits.01xz.net/wiki/Count_clock) HDLbits-Counter Clock

```
module top_module(  
    input clk,  
    input reset,  
    input ena,  
    output pm,  
    output [7:0] hh,  
    output [7:0] mm,  
    output [7:0] ss);  
  
    wire ena_ss, ena_mm, ena_hh, ena_pm;  
    assign ena_ss = ena;  
    assign ena_mm = ena & ss==8'h59; //sec=59  
    assign ena_hh = ena_mm & mm==8'h59; //min,sec=59'59  
    assign ena_pm = ena_hh & hh==8'h11; //hhmmss 115959  
  
    always@(posedge clk)begin  
        if(reset) begin  
            ss[7:0]<=8'h0;  
        end  
        else if(ena_ss) begin  
            ss[3:0]<= (ss[3:0]==4'h9)?4'h0:ss[3:0]+4'h1;  
            ss[7:4]<= (ss[3:0]==4'h9)?(ss[7:4]==4'h5)?4'h0:ss[7:4]+4'h1:ss[7:4];  
        end  
        else begin  
            ss <= ss;  
        end  
    end  
  
    always@(posedge clk)begin
```

```

if(reset) begin
    mm[7:0]<=8'h0;
end
else if(ena_mm) begin
    mm[3:0]<= (mm[3:0]==4'h9)?4'h0:mm[3:0]+4'h1;
    mm[7:4]<= (mm[3:0]==4'h9)?(mm[7:4]==4'h5)?4'h0:mm[7:4]+4'h1:mm[7:4];
end
else begin
    mm <= mm;
end
end

```

```

always@(posedge clk)begin
    if(reset) begin
        hh[7:0]<=8'h12;
    end
    else if(ena_hh) begin
        hh[3:0]<= (hh[3:0]==4'h9)?4'h0:(hh[7:0]==8'h12)?4'h1:hh[3:0]+4'h1;
        hh[7:4]<= (hh[3:0]==4'h9)?4'h1:(hh[7:0]==8'h12)?4'h0:hh[7:4];
    end
    else begin
        hh <= hh;
    end
end

```

```

always@(posedge clk)begin
    if(reset) begin
        pm<=1'b0;
    end
    else if(ena_pm) begin
        pm <= ~pm;
    end
    else begin
        pm <= pm;
    end
end

```

```

endmodule

```